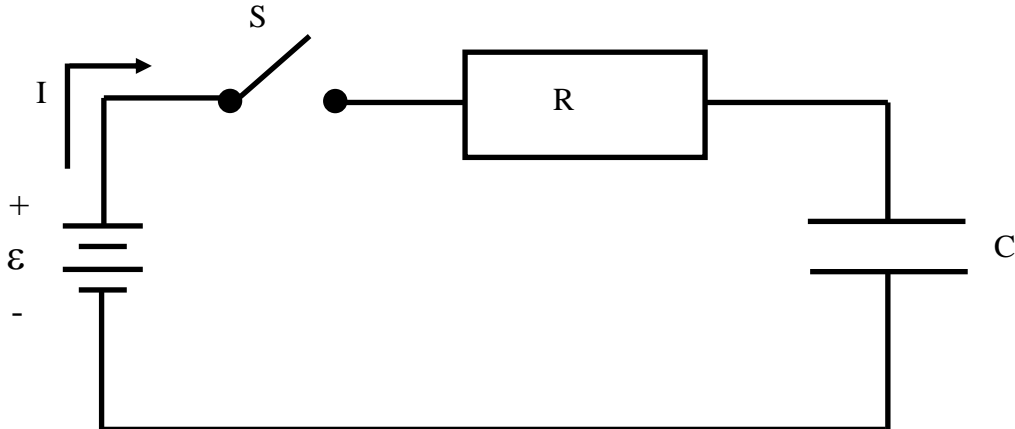


## RC Circuits

### I. Charging A Capacitor

#### A. Before Switch Is Closed: $t < 0$ s

##### 1. The Circuit



##### 2. Current Flowing In Circuit – $I_0$ .

##### 3. Voltage Across The Resistor – $V_{R0}$ .

Using Ohm's law, we have that


##### 4. Charge On The Plates Of The Capacitor – $Q_0$ .

In our problem, we will assume that no charge has been left on the capacitor's plate from a previous charging event.

##### 5. Voltage Across The Capacitor – $V_{c0}$ .

Using the definition of capacitance, we have

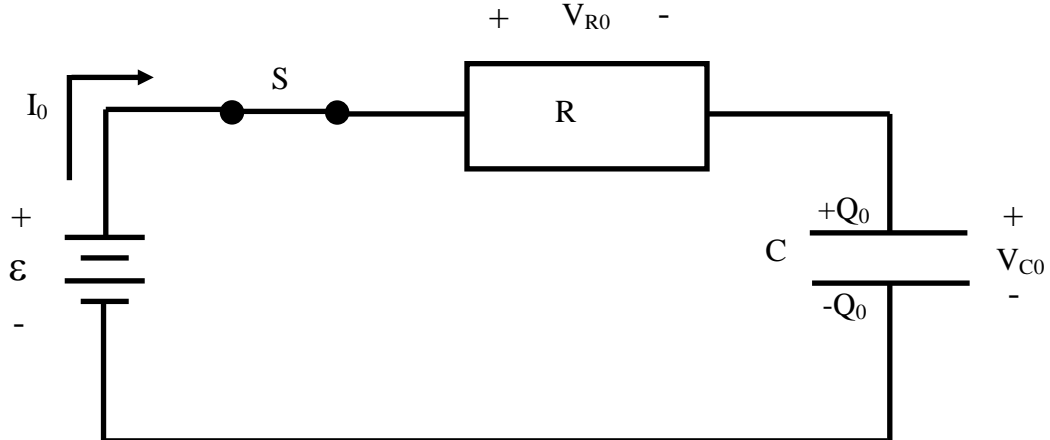**B. Immediately After Closing The Switch:  $t = 0$  s**  
**1. The Circuit**



**2. Charge On The Plate's Of The Capacitor's –  $Q_0$**

Because charged particles like electrons do not travel at infinite speeds, it will take at least a small finite amount of time for these particles to travel through the circuit and accumulate/leave the plates of the capacitor.

Thus, we have the following important condition for any RC circuit

The charge on a capacitor cannot change instantaneously (i.e. the function must be continuous).

In our particular problem, this corresponds to



**3. Voltage Across The Capacitor –  $V_{C0}$**

Since the voltage across a capacitor is directly proportional to the charge on the plates of the capacitor, our previous work can be restated as follows.

The voltage across a capacitor can not change instantaneously (i.e. the function must be continuous).

Thus, we have

**4. Voltage Across The Resistor –  $V_{R0}$**


Since our capacitor initially acts as a short circuit, we have by Kirchhoff's voltage law that

**5. Current Flowing In The Circuit –  $I_0$**

Using Ohm's Law, we have

**C. After Switch Has Been Closed For A Long Time:  $t \rightarrow \infty$  s**

**1. The Circuit**

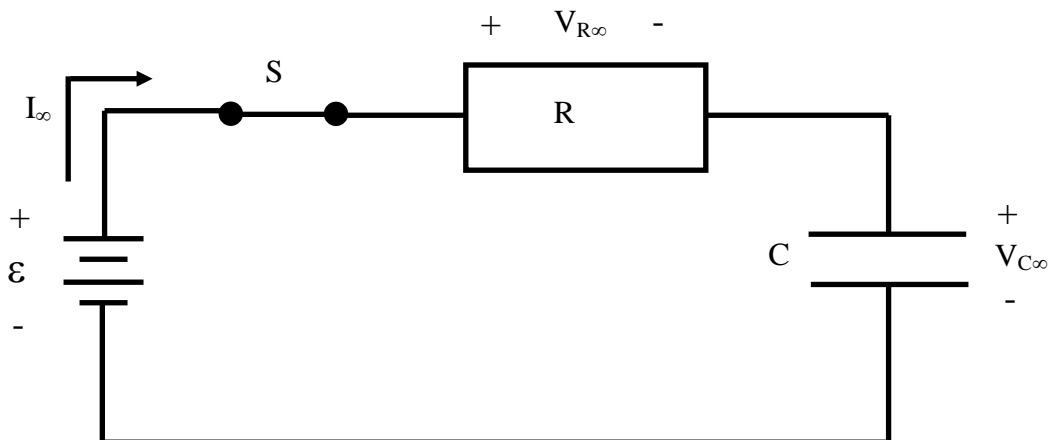

**2. Current Flowing In The Circuit -  $I_{\infty}$**

As charge increases on the capacitor plates, it becomes harder for new charge carriers to move between the plates. Eventually, the current flowing through the circuit will become **ZERO**.

Thus, we have the following important relationship:

a charging capacitor will eventually become an **OPEN** circuit.

**3. Voltage Across Resistor -  $V_{R\infty}$**

Using Ohm's Law, we have

**4. Voltage Across The Capacitor -  $V_{C\infty}$**





By Kirchhoff's Voltage Law, we have

**5. Charge On The Plates Of The Capacitor -  $Q_{\infty}$**

From the definition of capacitance, we know that

**D. Graphical Results For A Charging Capacitor**

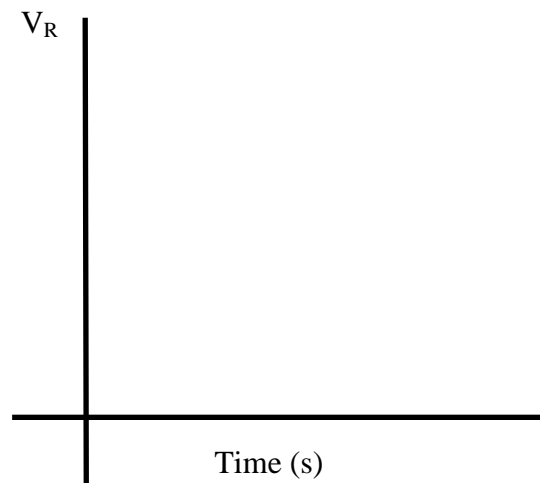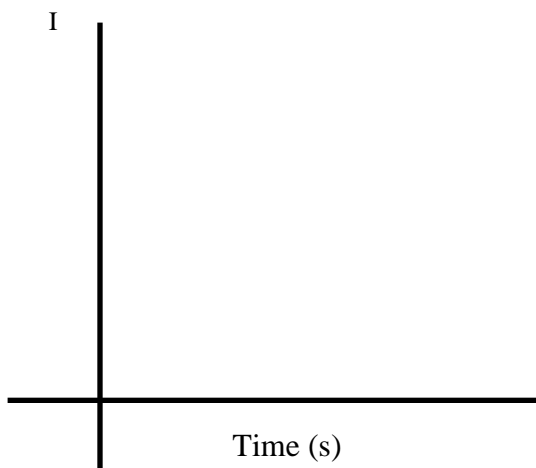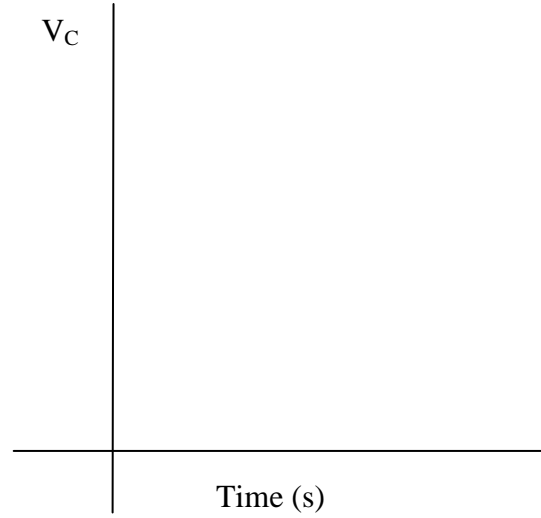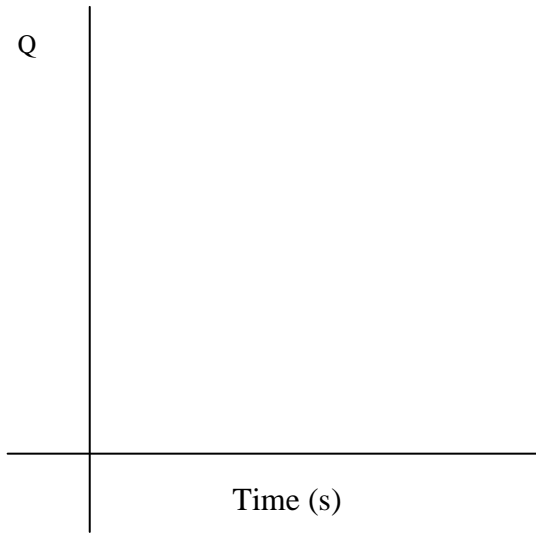1. We plot our three points for each graph that we found in parts A, B, and C.
2. On each graph, we can connect our points from parts B and C by realizing that the graphs must be continuous and that they are limited by the values found in part C.



$$I(t) = I_0 e^{-\left(\frac{t}{\tau}\right)} = \frac{\varepsilon}{R} e^{-\left(\frac{t}{\tau}\right)}$$

$$V_R(t) = V_{R \max} e^{-\left(\frac{t}{\tau}\right)} = \varepsilon e^{-\left(\frac{t}{\tau}\right)}$$

$$Q(t) = Q_{\max} \left( 1 - e^{-\left(\frac{t}{\tau}\right)} \right) = \varepsilon C \left( 1 - e^{-\left(\frac{t}{\tau}\right)} \right)$$

$$V_C(t) = V_{C \max} \left( 1 - e^{-\left(\frac{t}{\tau}\right)} \right) = \varepsilon \left( 1 - e^{-\left(\frac{t}{\tau}\right)} \right)$$

### E. RC Time Constant

The time it takes to charge a capacitor depends on the resistance and capacitance of the circuit.