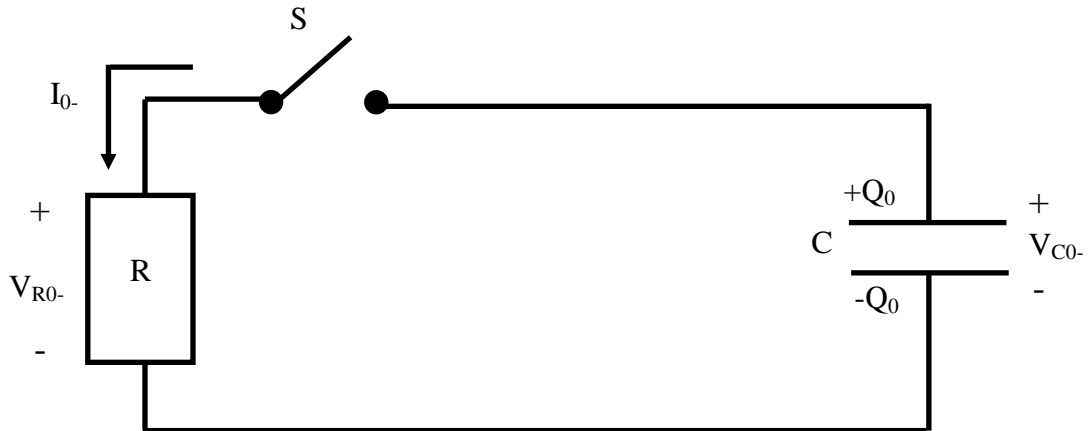


## RC Circuits II

### II. Discharging A Capacitor

#### A. Before Switch Is Closed: $t < 0$ s

##### 1. The Circuit



##### 2. Current Flowing In Circuit – $I_0$ .

Since we have an open circuit, we know that

##### 3. Voltage Across The Resistor – $V_{R0}$ .

Using Ohm's law, we have that

##### 4. Charge On The Plates Of The Capacitor – $Q_0$


In our problem, we will assume that the capacitor's plates have already been charged to an amount  $Q_0$

**5. Voltage Across The Capacitor –  $V_{C0}$ .**

Using the definition of capacitance, we have

**B. Immediately After Closing The Switch:  $t = 0$  s**

**1. The Circuit**

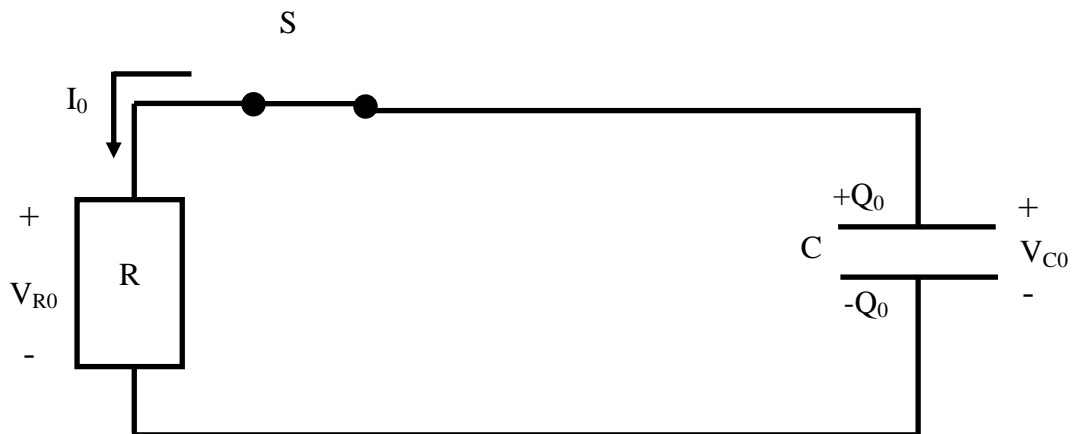

**2. Charge On The Plate's Of The Capacitor's –  $Q_0$**

**3. Voltage Across The Capacitor –  $V_{C0}$**

**4. Voltage Across The Resistor –  $V_{R0}$**

By definition of parallel circuits, we have

**5. Current Flowing In The Circuit –  $I_0$**

Using Ohm's Law, we have

**C. After Switch Has Been Closed For A Long Time:  $t \rightarrow \infty$  s**

1. As current flows through the circuit, the charge on the plates of the capacitor will decrease until the capacitor plates are neutral.

**2. Voltage Across Capacitor -  $V_{C\infty}$**

**3. Voltage Across Resistor -  $V_{R\infty}$**





By definition of parallel circuits, we have

**4. Current In the Circuit -  $V_{C\infty}$**

By Ohm's Law, we have

**D. Graphical Results For A Discharging Capacitor**

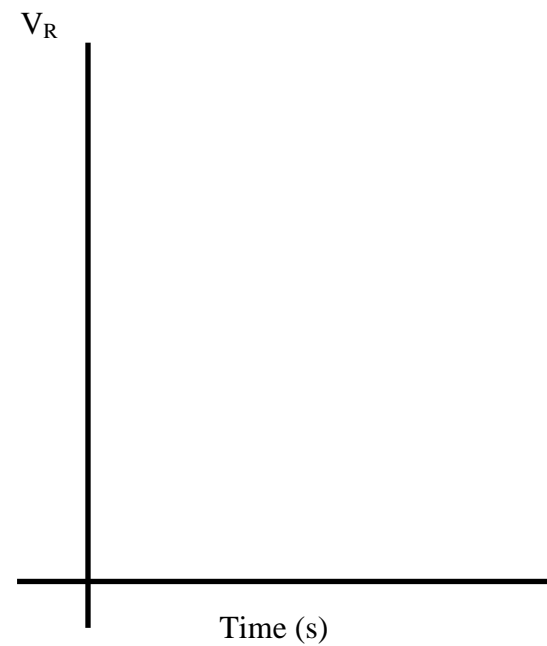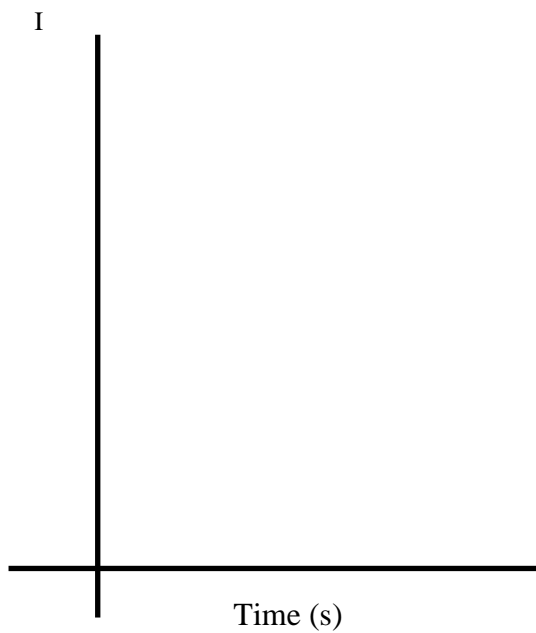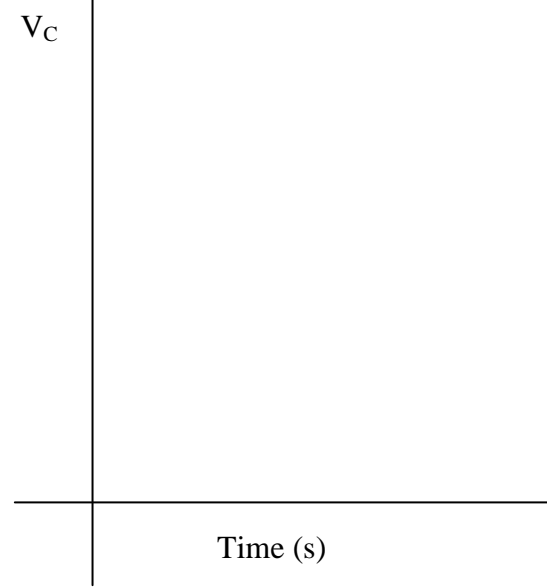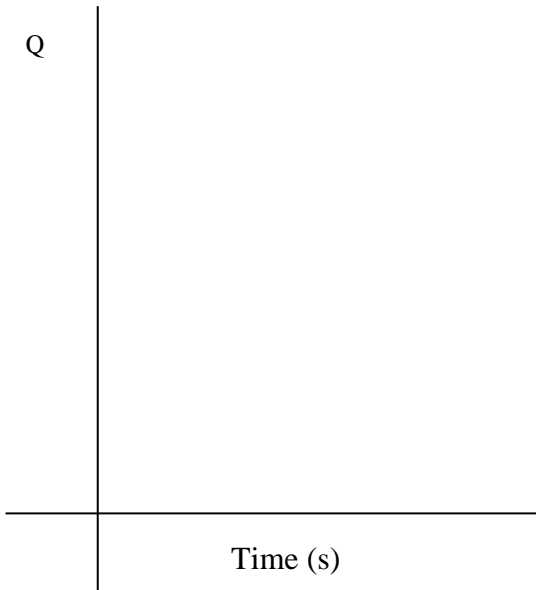1. We plot our three points for each graph that we found in parts A, B, and C.
2. On each graph, we can connect our points from parts B and C by realizing that the graphs must be continuous and that they are limited by the values found in part C.



$$I(t) = I_0 e^{-\left(\frac{t}{\tau}\right)} = \frac{\varepsilon}{R} e^{-\left(\frac{t}{\tau}\right)}$$

$$V_R(t) = V_{R0} e^{-\left(\frac{t}{\tau}\right)} = \frac{Q_0}{C} e^{-\left(\frac{t}{\tau}\right)}$$


$$Q(t) = Q_0 e^{-\left(\frac{t}{\tau}\right)}$$

$$V_C(t) = V_{C0} e^{-\left(\frac{t}{\tau}\right)}$$

$$\tau = RC$$

### Capacitor Problem

You are given the following RC circuit

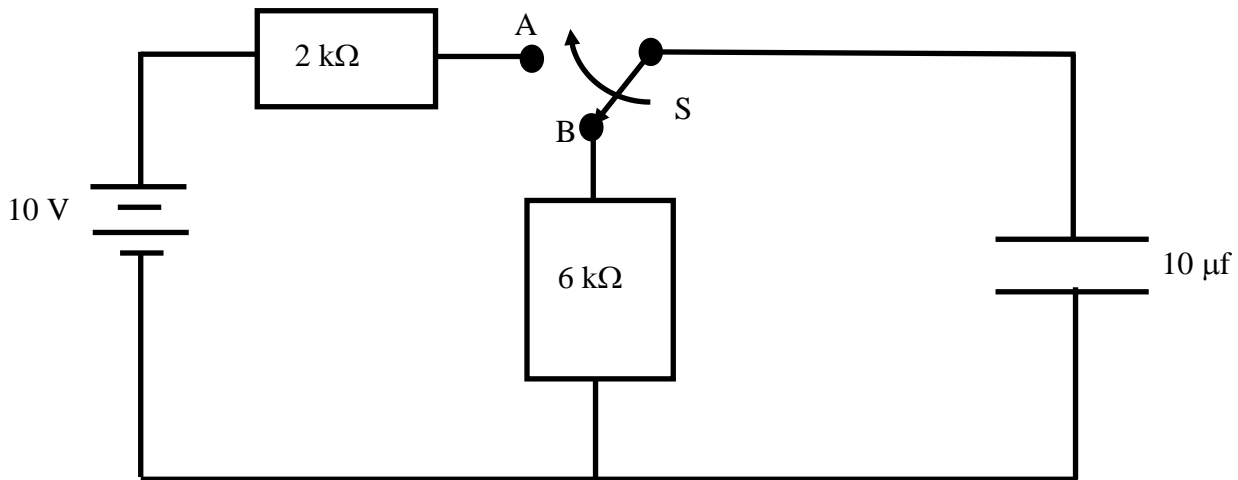

- A. What is the time constant when the switch is set to position A (“charging”)?
  
  
  
  
  
  
  
  
  
  
- B. What is the initial current through the 2 kΩ resistor when we begin charging the capacitor?
  
  
  
  
  
  
  
  
  
  
- C. What is the maximum voltage across the capacitor after charging?

- D.** What is the maximum charge on the plate of the capacitor?
- E.** What is the voltage 15 ms after the capacitor begins to charge?
- F.** What is the time constant for the switch in position B (“discharging”)?
- G.** If the capacitor is initially charged to 4 Volts, what is its voltage 20 ms after the switch is thrown to position B?